



USAID
FROM THE AMERICAN PEOPLE

SARI / Energy

Measurement of Power in single and 3-Phase Circuits

by : N.K.Bhati

A specifically designed programme for

Da Afghanistan Breshna Sherkat (DABS)
Afghanistan



USAID
FROM THE AMERICAN PEOPLE

SARI / Energy

Areas Covered Under this Module

- 1. Power in ac circuits**
- 2. Measurement of power and Energy in single and three circuits**
- 3. Two and three wattmeter methods in balance and unbalance circuits**

Power in ac circuits.. a quick recap

- Power per phase is

$$P = V_p I_p \cos(\phi)$$

- Power for all three phases is

$$P = 3 V_p I_p \cos(\phi) \text{ or}$$

$$P = V_1 I_1 \cos(\phi_1) + V_2 I_2 \cos(\phi_2) + V_3 I_3 \cos(\phi_3)$$

- Since for a balanced load the power is constant

$$P(t) = 3 V_p I_p \cos(\phi) \text{ also}$$

- Power in Terms of Line Quantities

$$P = \sqrt{3} V_L I_L \cos(\phi)$$

Power in ac circuits.. a quick recap

- Total supply Volt Amps product (VA) is

$$VA = \sqrt{3} V_L I_L$$

- Reactive power Q is the Quantity making up the difference between VA and Power

$$Q = \sqrt{3} V_L I_L \sin(\phi)$$

- Thus $VA^2 = P^2 + Q^2$
- Q is a measure of the energy storage capability of the circuit
- For the greatest Power per amp of supply the Power Factor should be Unity and Q should be zero

Power in ac circuits.. a quick recap

- Balanced conditions
 - All 3 phase voltages (rms) are equal
 - All 3 phase currents (rms) are equal
 - Phase angle ϕ is the same for all 3 phases
 - 120 degrees electrical between voltages
- Balanced conditions give no neutral current
- Instantaneous Power is constant
- Reactive power Q when ϕ is not zero reduces utilisation of current



Measurement of Power and Energy

- *Power is the rate at which energy is transformed.*
- *Measurement of active power : by wattmeter
(an indicating type Instrument)*
- *Measurement of energy :
by Energy meter
(an integrating type instrument)*

Wattmeter

- Electro-dynamic or Dynamometer type.
- Induction type or Electromechanical meter
- Thermal type
- Electronic instruments

Electrodynamic wattmeter

- The device consists of a pair of fixed coils, known as *current coils*, and a movable coil known as the *potential coil*.
- The current coils connected in series with the circuit, while the potential coil is connected in parallel.
- On analog wattmeters, the potential coil carries a needle that moves over a scale to indicate the measurement.
- A current flowing through the current coil generates an electromagnetic field around the coil. The strength of this field is proportional to the line current and in phase with it.
- On an ac circuit the deflection is proportional to the average instantaneous product of voltage and current, thus measuring true power ($P = v.i$)




Digital watt meters

- Based on Analog or digital techniques of measurement.
- Measures true rms V, I, Watts.
- Low cost , high accuracy



Measurement of Power in Single Phase AC Circuits

- Single wattmeter method

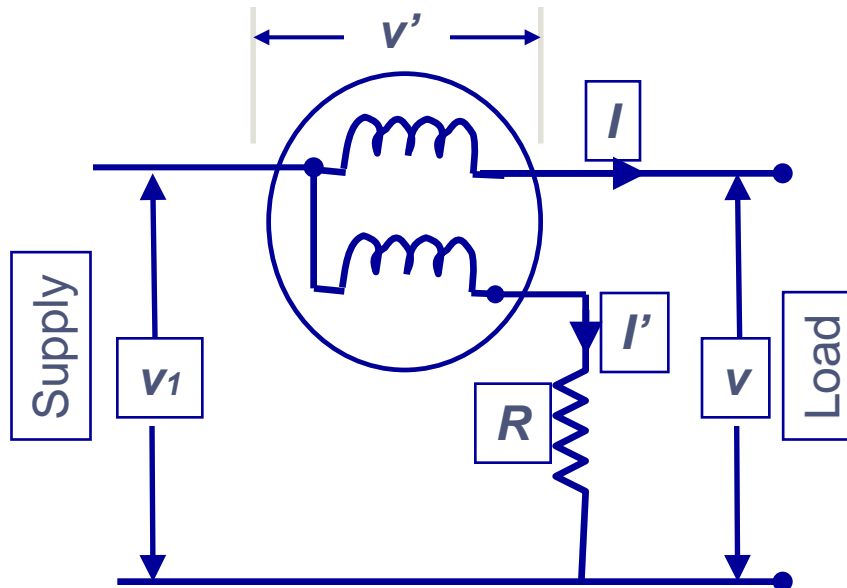


Three or Two Wattmeter Method

- BLONDEL'S THEOREM
 - In an N-wire circuit, only (N-1) watt meters are required to measure the power.
- 2 Wattmeter method measures the power of 3 phase star or delta connected balanced / unbalanced loads
- 3 wattmeter method is used for 4 wire circuits , like LT or HT circuits

Measurement of Power in 3 Phase Circuits


- 3-Wattmeter Method
 - The method is applicable in 3-phase 4 wire circuits, Works well for balanced and unbalanced loads.
 - In 3phase 3 wire circuits an artificial neutral is created through 3 equal high resistances connected in star.
 - In case of low voltage circuits three potential coils may be connected to form a common star.

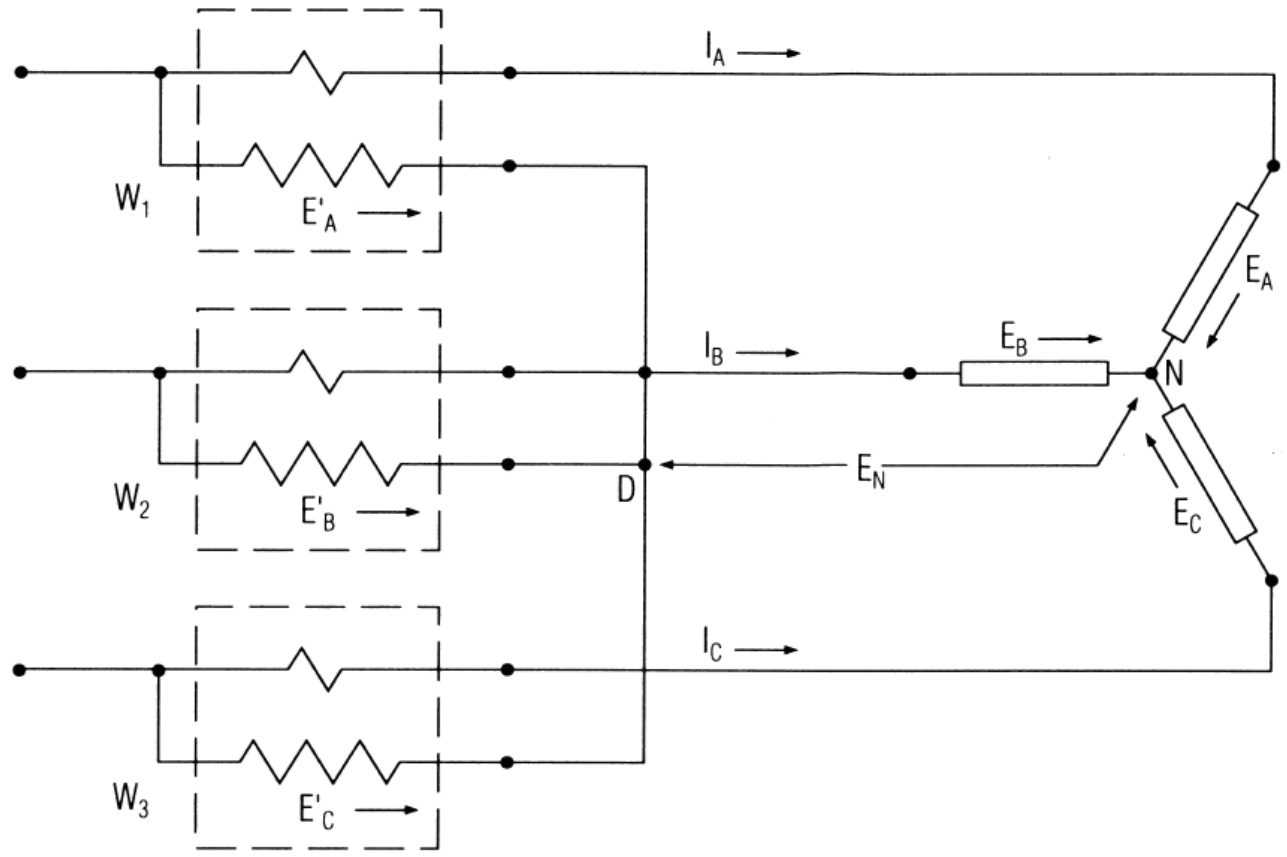3 phase power Measurement : 3 Wattmeter Method



Total power of load circuit, $P = W1 + W2 + W3$


Two Wattmeter Method in Star Circuit

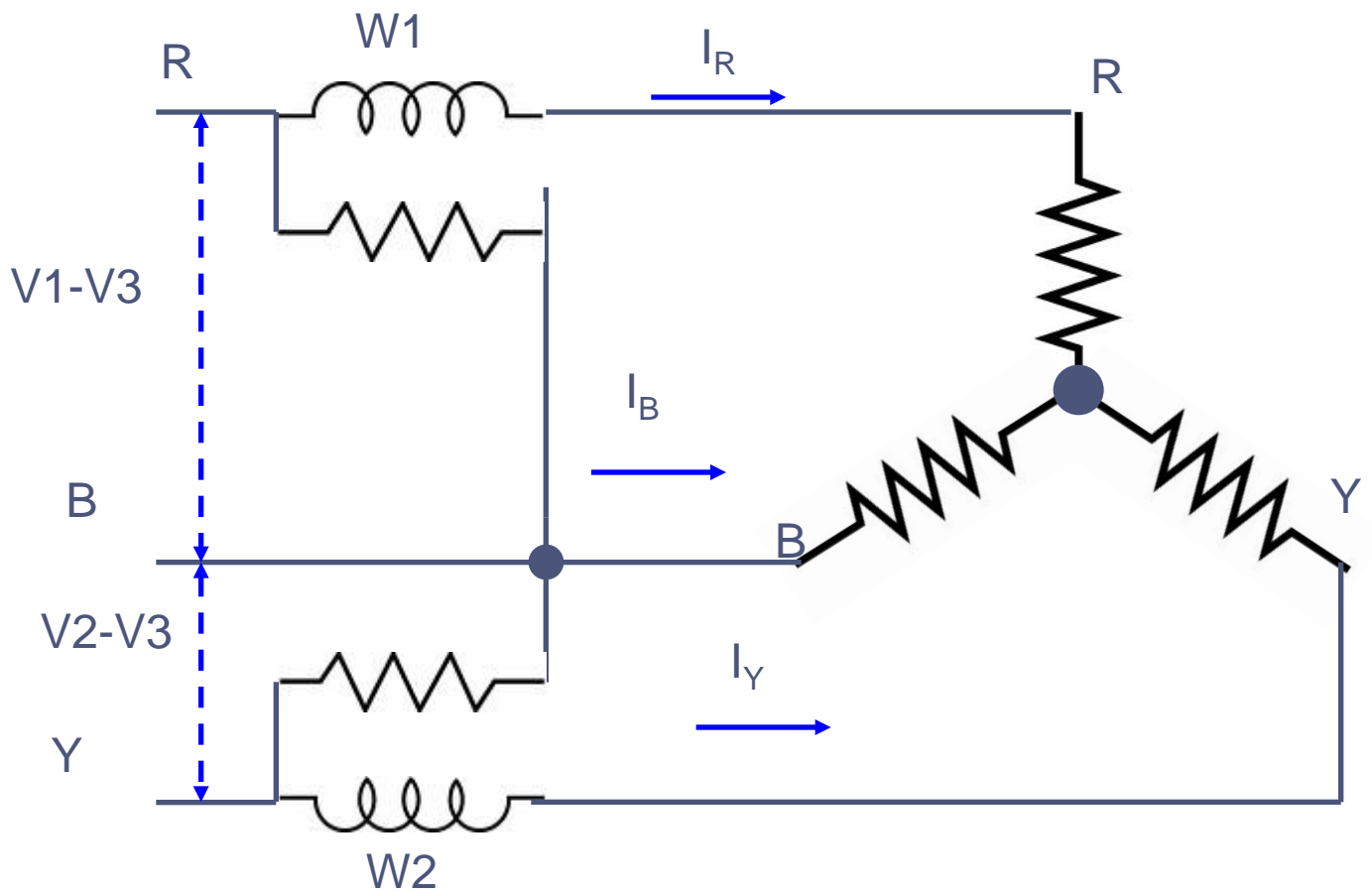

Total average power $P = W1 + W2$




Two wattmeter in Delta circuit

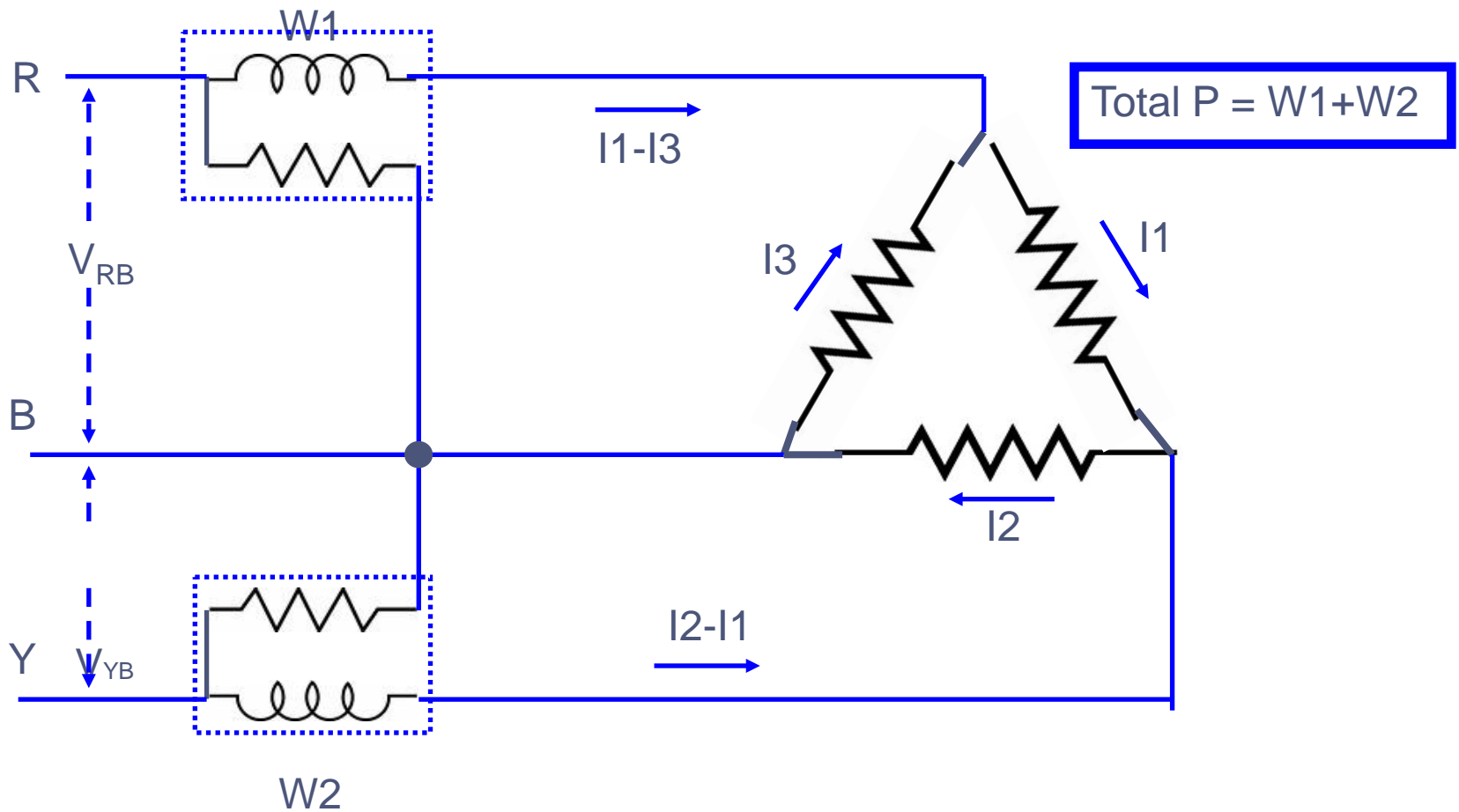

3 Φ 3 W Method

Vector Representation

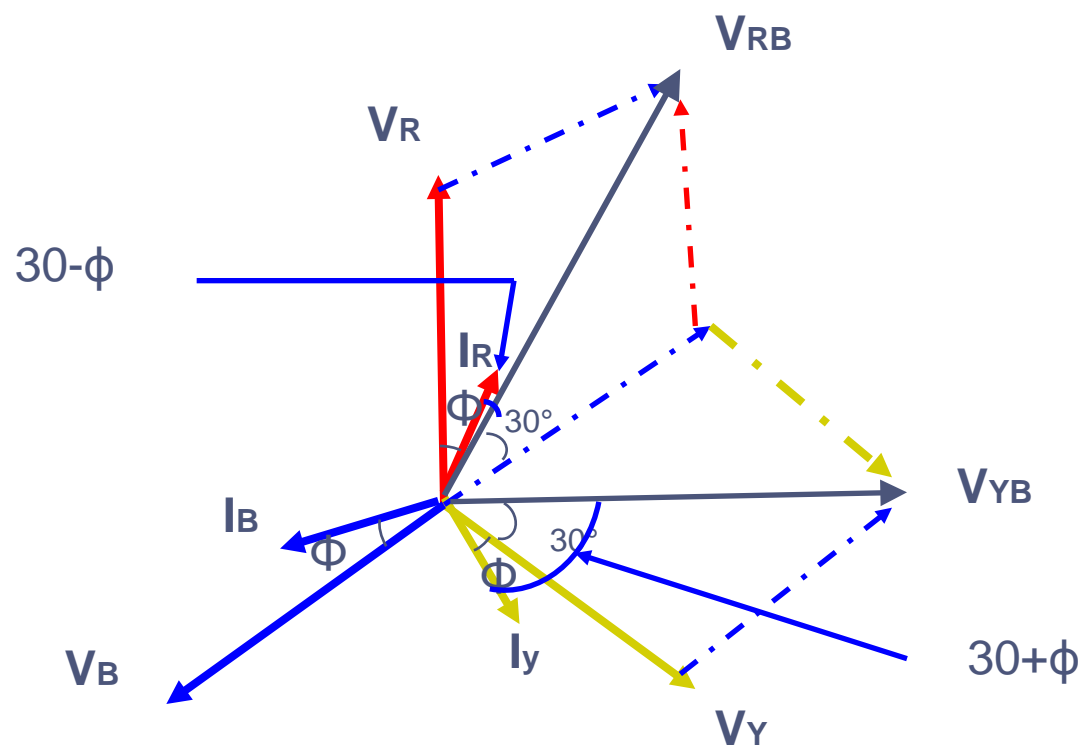



3 Φ 3 W Method

Total Power = sum of two watt meter readings

$$W1 + W2$$

$$= V_{rb}.I_r. \cos (30^\circ - \Phi) + V_{yb}.I_y. \cos (30^\circ + \Phi)$$

$$= V_L I_L \times 2 \cos 30^\circ \cos \Phi$$

$$= \sqrt{3} V_L I_L \cos \Phi$$

$$= 3VI \cos \Phi$$

= True power of load

(This is true for any phase used as reference, as well for unbalanced loads also.)



Measurement of energy

- Power integrated over time gives energy
- All energy meters do this.
 - In EM induction type meters, speed of rotation of the disk is proportional to power, and integrated by use of gear trains and mechanical counters.
 - In electronic (analog type meters), power is converted to a proportional frequency or pulse rate, and integrated by use of EM counters.
 - In Digital Energy meters, power is continuously integrated in digital domain by processor to get energy and is also converted to a proportional frequency or pulse rate for calibration /testing purpose.

Connections

- **Classification of Energy Meters**
- **Connection of 3- \emptyset , Whole Current Meter**
- **Connection of 3- \emptyset , LT-CT Operated Meter**
- **Connection of HT, 3P4W Meter**
- **Connection of HT, 3P3W Meter**
- **Connection of Single phase 2E Meter**
- **Precautions while connecting Meters**
- **Connection check for 3P4W and 3P3W Meters**

Classification of Energy Meters

Metering Point

Network Section	HV/LV	3/4 wire
Grid	HV 275/400kV	3 wire
Secondary Trans. Primary Dist.	HV 33/11kV	3 wire
Local Dist.	LV 400V	3 wire
	400V	4 wire
	230V (1Ø)	2 wire

HV = High Voltage, LV = Low Voltage

End Application

- Domestic
- Commercial
- Industrial (Small, Medium, Large)
- Grid Metering
- Billing or Check Meter
- Nature of Load (Traction, Induction furnace)




Technical

- Three phase or Single phase
- HT, LT or Whole Current
- If HT then 3P4W or 3P3W
- Basic Voltage (V_b)
- Basic Current (I_b)
- Max Current (I_{max}) for long range meter
- Accuracy class (0.2s, 0.5s, 1.0, 2.0)



Single Phase Meter Connection

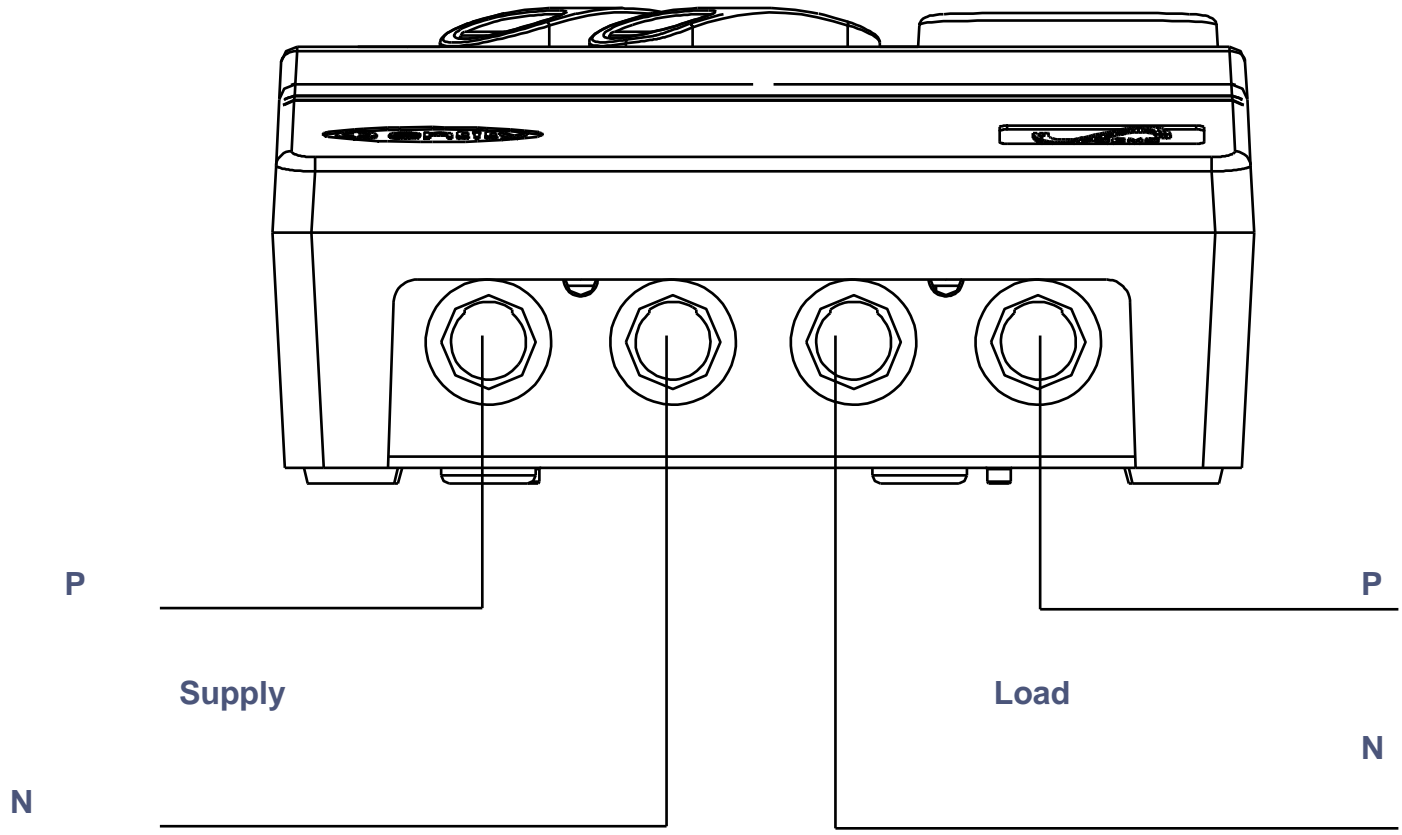

Precautions while Connecting Meter




- Use cable size as per the current rating
- Remove insulation exactly equal to terminal depth.

13mm Diameter Cable

11mm Diameter Cable


Whole Current Meter

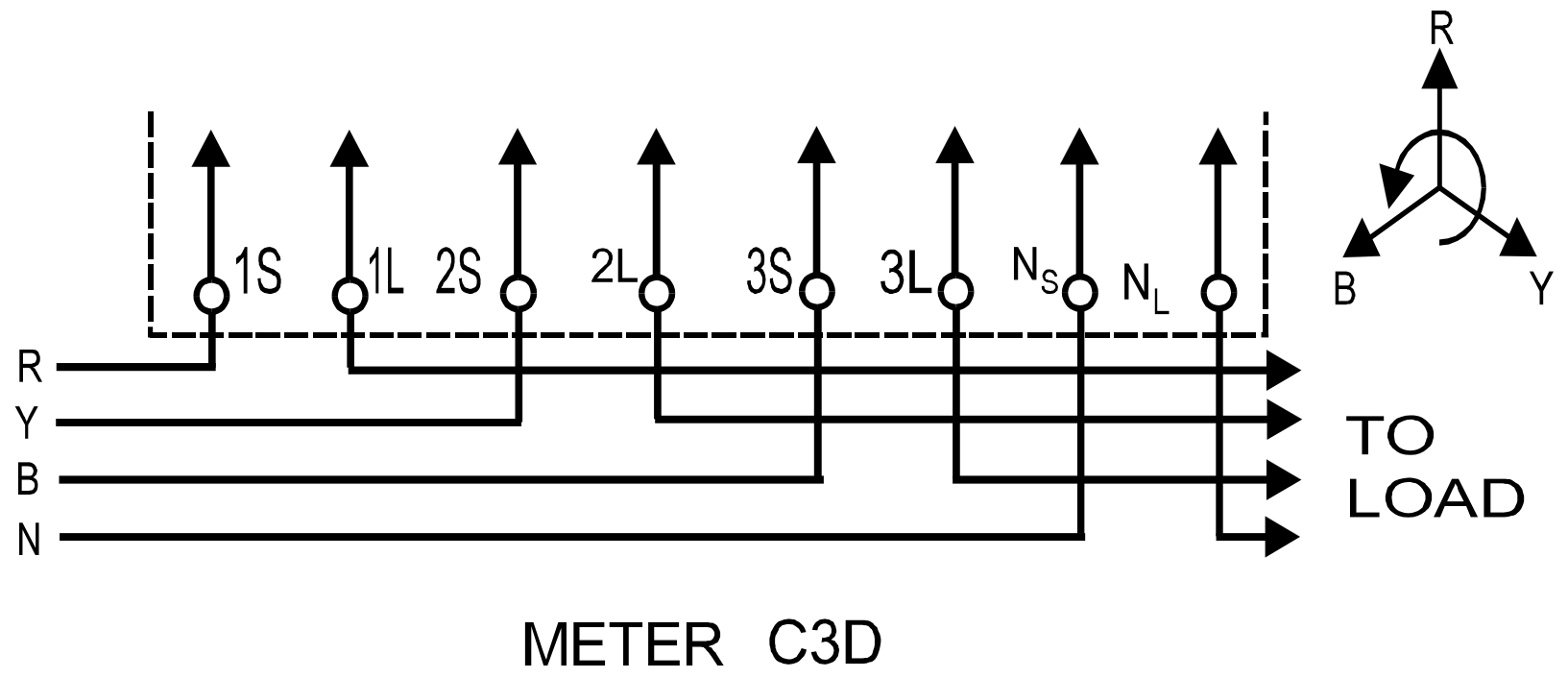

LT-CT 3P4W Meter

CT secondary rating: 1A or 5A

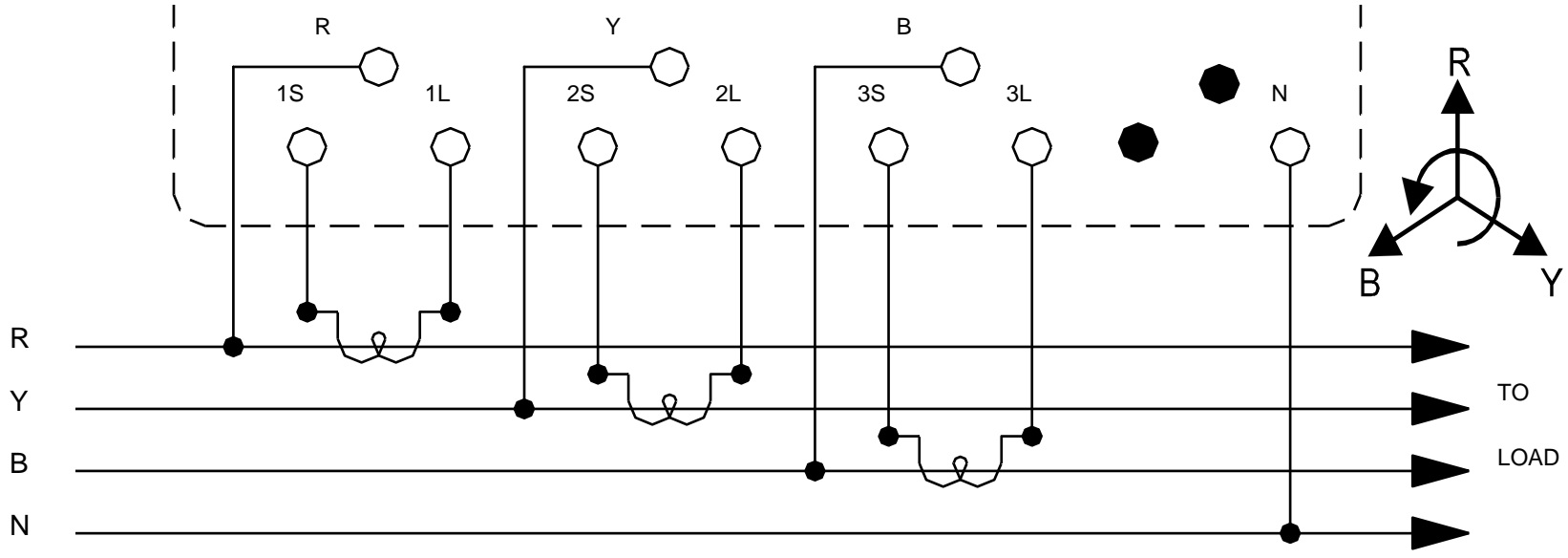CT Primary rating: can be commissioned to any one of the standard values




C3T Type Meter



HT 3P4W Meter

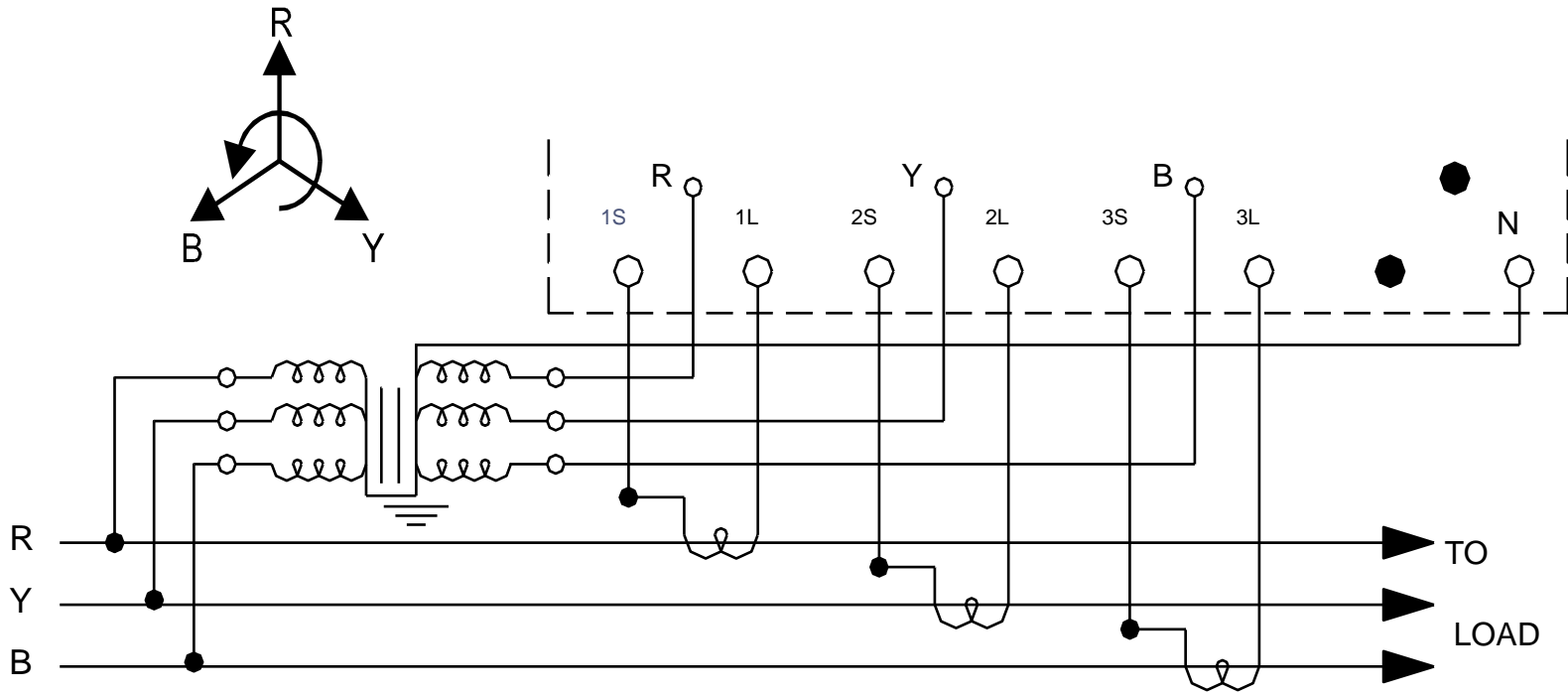
Voltage rating: $110/\sqrt{3}$ V, Sec. current rating: 1A or 5A
Primary voltage and current range can be commissioned to any one of standard values.





HT 3P3W Meter

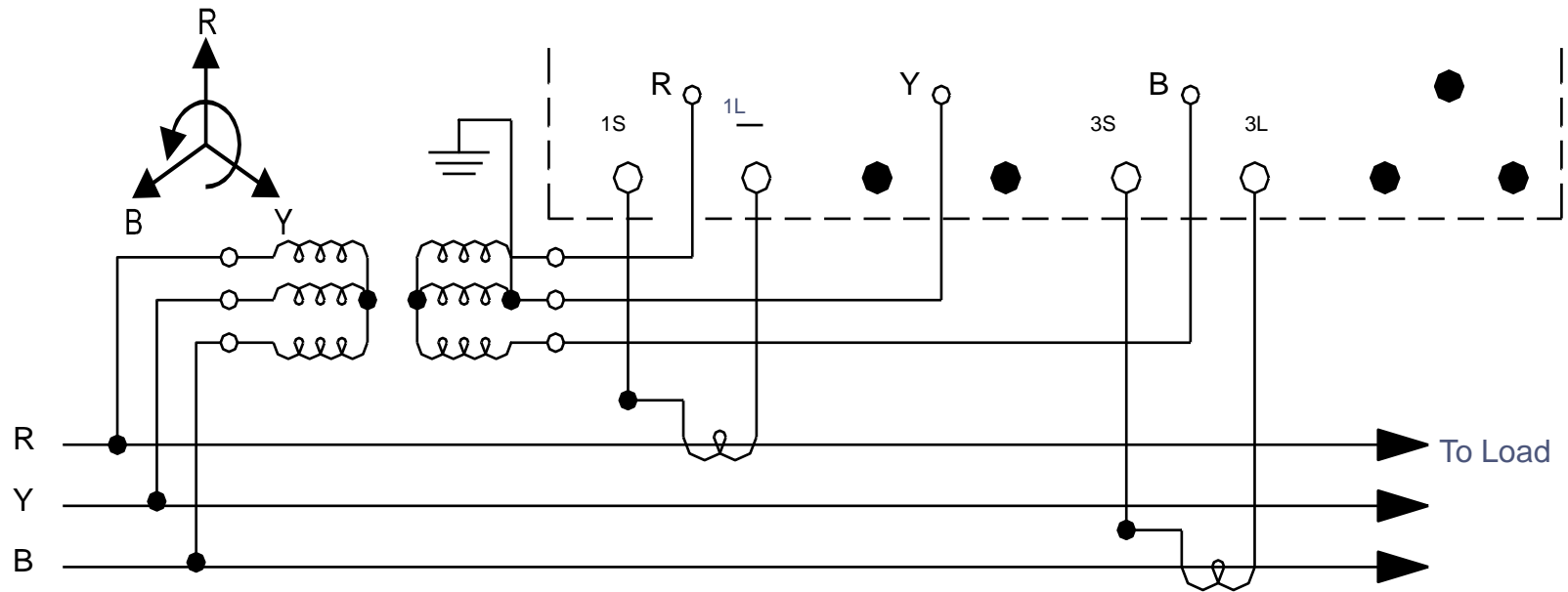Voltage rating: 110V, Sec. Current rating: 1A or 5A
Primary voltage and current range can be commissioned to any one of standard values.




C3V Type Meter

Precautions while Connecting CT-Operated Meter

- Meter must be connected using Test Terminal Block (TTB)
- CT Secondary must kept shorted until meter is connected.
- Under no case CT secondary shall be open, it may result in high voltage flash over or CT burst.


TTB

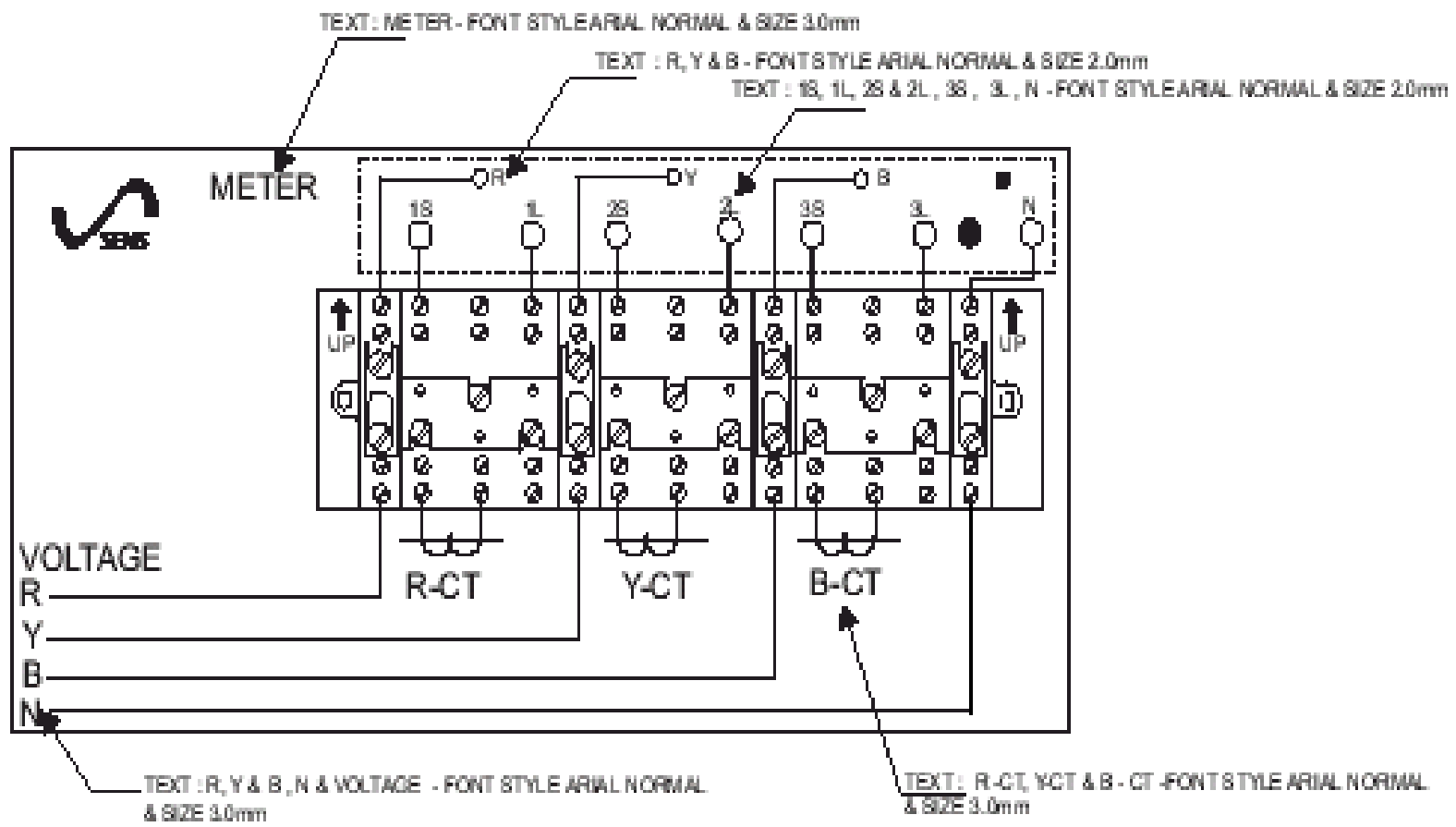

PRINTING DETAILS

Meter Connection Check


Vector diagram 3P4W – Connection Check

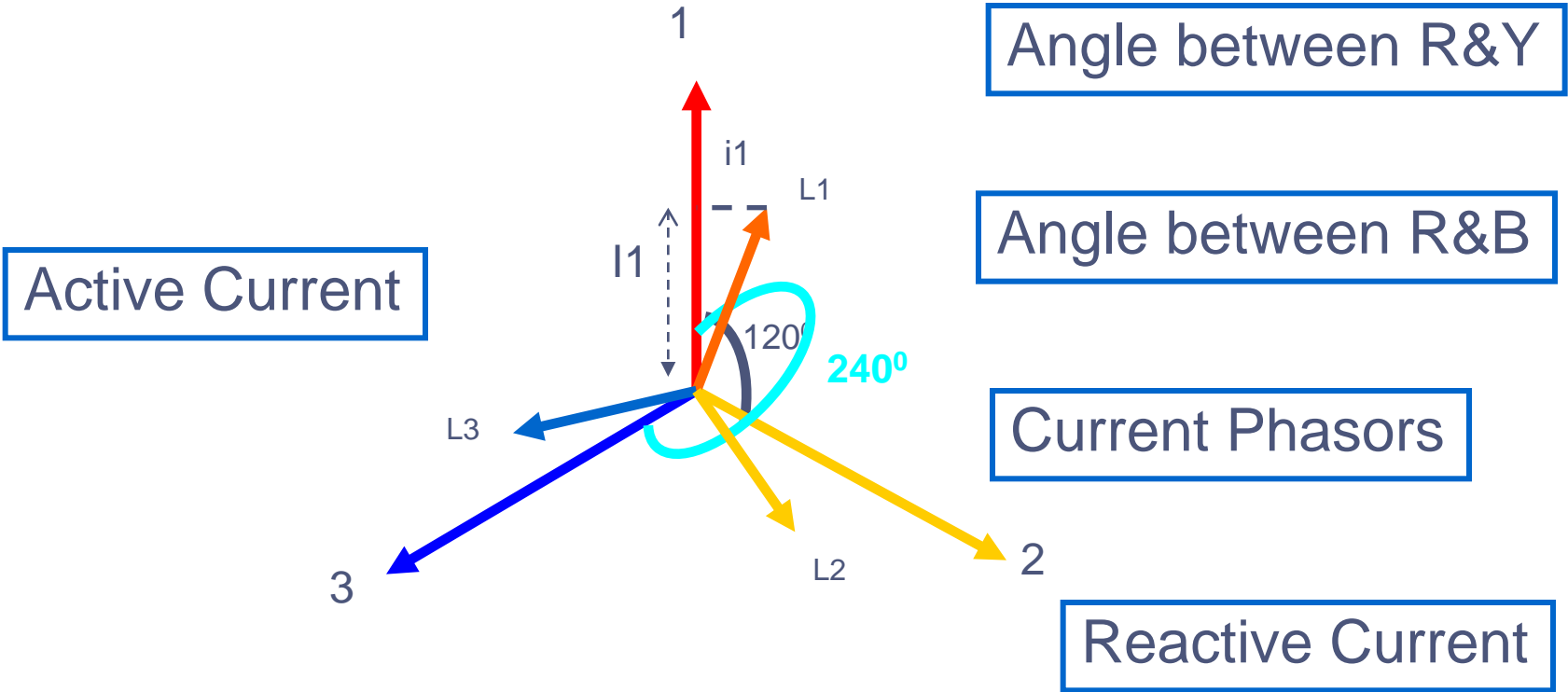

Connection Check for 3P4W Meter

- Read V1, V2, V3, L1, L2, L3, I1, I2, I3 , A2, A3 from the meter
- Draw the vector diagram as shown. The phase sequence is find out by reading angle A2 and A3 which have value 120° & 240° respectively for RYB (forward phase sequence) and 240° & 120° for RBY (reverse phase sequence).

3P3W Meter – Connection check

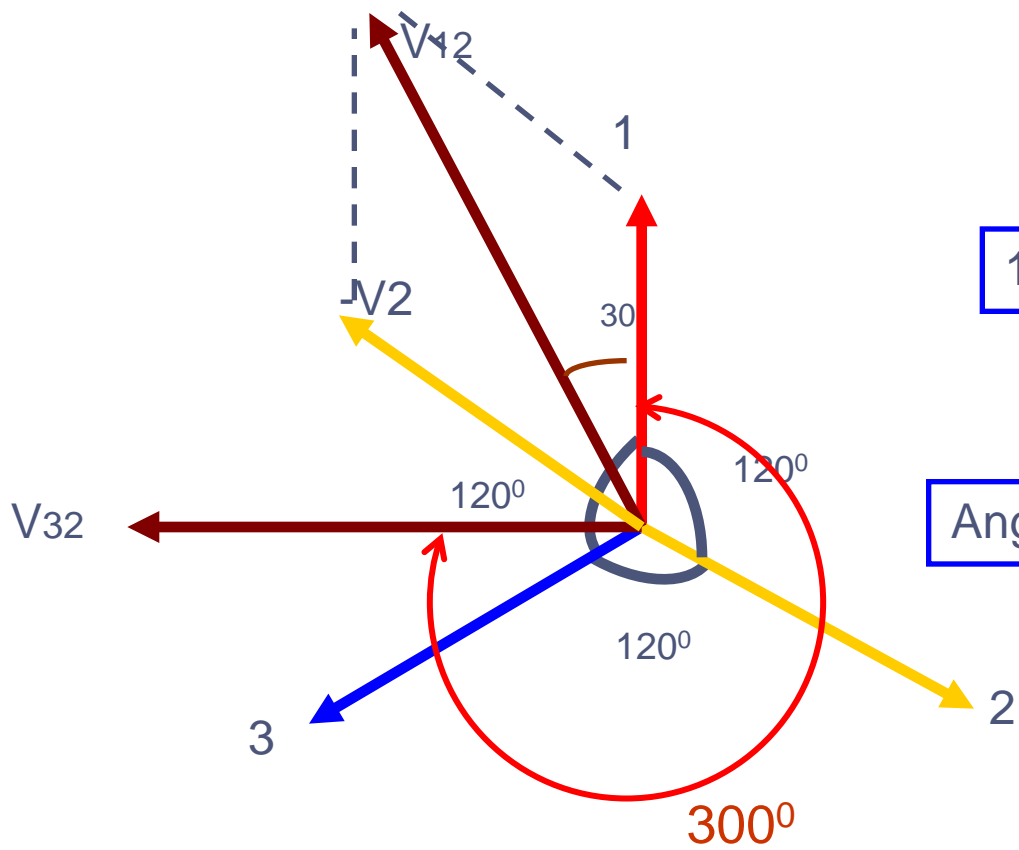

1,2,3 phase voltages

12,23,31 – Line voltages

Angle Between V12 and V31

Connection Check for 3P3W Meter

- Read $V1$, $V3$, $L1$, $L3$, $I1$, $I3$, $i1$, $i3$ etc.
- Draw the vector diagram as shown.
- The phase sequence is find out by reading angle $A3$ which will have value 300° for RYB (forward phase sequence) and 60° for RBY (reverse phase sequence).

Question Please?

Thank you